

Exam 1 Practice Problems Solution

Note: The actual exam might have very different problems/questions and might be of a different length. The following problems are intended for you to practice in addition to studying what is in the slides and practicing with the examples in them.

Problem 1:

Given the following function:

$$\text{Out} = (ab)' + cd' + e'f$$

- a. Write the expression representing the pull-up network (PUN)

$$\begin{aligned}\text{Out (inputs')} &= (a'b')' + c'd + ef \\ &= (a+b) + c'd + ef\end{aligned}$$

- b. Write the expression representing the pull-down network (PDN)

$$\begin{aligned}\text{Out}' &= [(ab)' + cd' + e'f]' \\ &= (ab) (cd')' (e'f)' \\ &= ab (c'+d) (e+f)\end{aligned}$$

Problem 2:

We would like to design a circuit that outputs the remainder of dividing its input by 3 (i.e., %3).

- a. Fill out the following truth table representing the circuit where X is the input and Y is the output.

X ₂	X ₁	X ₀	Y ₁	Y ₀
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

- b. Write the SoP equation for each output bit in terms of the input bits. Do not minimize.

$$Y_1 = X_2'X_1X_0' + X_2X_1'X_0$$

$$Y_0 = X_2'X_1'X_0 + X_2X_1'X_0' + X_2X_1X_0$$

Problem 3:

You are to design a component that takes a 3-bit input and outputs the quotient of the division of the input by 3 (this output is 2 bits).

X_2	X_1	X_0	Y_1	Y_0
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0


$$Y_1 = X_2X_1X_0' + X_2X_1X_0$$

$$Y_0 = X_2'X_1X_0 + X_2X_1'X_0' + X_2X_1'X_0$$

 - a. Draw the transistor-level circuit for both output bits (do not minimize)


Y_1 PUN:

$$Y_1 (\text{inputs}') = x_2' x_1' x_0 + x_2' x_1' x_0'$$




Y_0 PUN:
 
$$Y_0 (\text{inputs}') = x_2 x_1' x_0' + x_2' x_1 x_0 + x_2' x_1 x_0'$$



 - b. Draw the gate-level circuit for the component using only NOR gates (start from the SoP and do not minimize)



Then:

- Add 2 bubbles (NOT gates) at the output of every OR gate
- Replace both (OR+NOT) with a NOR
- Add 2 bubbles at the input of every AND gate
- Replace the 5 (NOT+AND) with a NOR
- Replace remaining bubbles/NOT gates with a 2-input NOR gate having its inputs connected

Problem 4:

Write the 6-bit 2's complement representation of the following decimal numbers:

- i. +7: 000111
- ii. -7: 111001

Problem 5:

Convert the IEEE Single Precision Floating Point 0x42F20000 to binary then to its equivalent decimal value.


1 Sign Bit	8 Biased Exponent Bits	23 Mantissa Bits
0	100 0010 1	111 0010 0000 0000 0000 0000

Decimal value:

$$+1.111001_2 \times 2^{133-127} = 1111001_2 = 121$$

Problem 6:


Draw the design of a 4:1 mux having inputs in0 (top) to in3 (bottom) and select bits s1s0 using 2:1 muxes. Clearly show where each input goes.

 

 
Problem 7:

Draw the Moore state diagram for the FSM with the following specification. The machine has a 1-bit input and a 1-bit output which is initially '0'.

- The output of this machine should become '1' if the last 3 out of 4 inputs were '1'.
- Once the output switches to '1', it should stay there until 2 consecutive inputs of '0' are received, then it turns '0'.



or

 **Problem 8:**

Convert the following C code into MIPS assembly while performing all necessary stack operations. Feel free to use any available registers.

```
int weirdMath(int a, int b) {
    int c = a + b;
    int d = doMagic(c); //function call located at label DO_MAGIC
    c = c + d;
    return c;
}
...
int x = weirdMath(1, 2);
```

```

WEIRD_MATH:    subiu $sp, $sp, 8
               sw $fp, 0($sp)
               sw $ra, 4($sp)
               addiu $fp, $sp, 4
               add $s0, $a0, $a1
               add $a0, $s0, $0
               jal DO_MAGIC
               add $v0, $s0, $v0
               lw $ra, 4($sp)
               lw $fp, 0($sp)
               addiu $sp, $sp, 8
               jr $ra
               ...

               li $a0, 1
               li $a1, 2
               jal WEIRD_MATH

```

Problem 9:

Add the necessary components and connections to our 6-instruction MIPS datapath to accommodate for the jr instruction.

